



University of Engineering & Management, Kolkata

Term - I Examination, August - September, 2021

Programme Name: B.Tech in Computer Science

Semester: 5th

Course Name: Analog Electronic Circuits

Course Code: ESC 502

Full Marks: 100

Time: 3 hours

GROUP A (20 Marks)

Answer the following questions. Each question is of 2 marks.

- | | | | |
|----|-------|--|---|
| 1. | i) | Define the Purpose of regulators in a circuits | 2 |
| | ii) | Describe the ripple factor of a full wave rectifier. | 2 |
| | iii) | Classify the types of filters used for ac to dc conversions. | 2 |
| | iv) | Relate the necessity of Amplifiers in Electronic devices | 2 |
| | v) | Classify the types of series and shunt regulators. | 2 |
| | vi) | Summarize the application of bias point in brief | 2 |
| | vii) | Explain the full form of Current gain in amplifier. | 2 |
| | viii) | Teach the functions of L and R in Filters | 2 |
| | ix) | Describe the equation for capacitive reactance | 2 |
| | x) | Relate the function of ripples in power supply. | 2 |

GROUP B (30 Marks)

Answer the following questions. Each question is of 5 marks.

- | | | | |
|-------|-----|--|---|
| 2. | i) | Describe the working principle of a Step UP Transformer with characteristic equations. | 5 |
| 3. | i) | Contrast the differences between filters and rectifiers. | 3 |
| | ii) | Explain whether a Rectifier can convert ac to dc or not. | 2 |
| 4. | i) | Summarize bias point. | 2 |
| | ii) | Classify the factors on which it depends on. | 3 |
| 5. A. | i) | Sketch the Ripple factor of a Full wave and bridge rectifier | 5 |

OR

- | | | | |
|-----------|------------|--|----------|
| B. | i) | Explain the operation of Load Line analysis. | 3 |
| | ii) | Memorize its Importance | 2 |
| | | | |
| 6. | A. | i) Relate the differences between IC regulators and L, and C filters. | 5 |

OR

- | | | | |
|-----------|-----------|---|----------|
| B. | i) | Contrast the differences between Load line and Q Point | 5 |
| | | | |
| 7. | A. | i) Sketch the diagram of a Shunt regulator and explain its operation | 5 |

OR

- | | | | |
|-----------|------------|---|----------|
| B. | i) | categorize positive and negative IC regulators. | 3 |
| | ii) | Contrast the differences between Pi and L filters | 2 |

GROUP C (50 Marks)

Answer the following questions. Each question is of 10 marks.

- | | | | |
|------------|------------|--|-----------|
| 8. | i) | Define the importance of Q point Biasing and explain its classifications. | 5 |
| | ii) | Interpret the circuit diagram of a Emitter bias circuit and explain its operation. | 5 |
| | | | |
| 9. | i) | Relate why emitter bias is called a self bias. | 5 |
| | ii) | Sketch the details of a self biasing circuit and explain its operation. | 5 |
| | | | |
| 10. | A. | i) Compare between Self bias and voltage divider bias. | 5 |
| | ii) | Illustrate the circuit diagram of a potential divider bias and explain its operation | 5 |
| | | | |
| OR | | | |
| B. | i) | Explain the superiority of Voltage divider bias over all other biasing techniques. | 5 |
| | ii) | Solve the purpose of use of Diodes in Rectifier circuits with suitable mathematical expression. | 5 |
| | | | |
| 11. | A. | i) Extract the full working principle of a Full wave rectifier with suitable diagram and explain the ripple factor. | 10 |

OR

- | | | | |
|---------------|------------|---|-----------|
| B. | i) | Illustrate Op amp based shunt Voltage regulator and explain its operation. | 10 |
| 12. A. | i) | Correlate between with and without op amp regulators. | 5 |
| | ii) | Describes the advantages of IC regulators in voltage regulation over series and shunt regulators. | 5 |

OR

- | | | | |
|-----------|------------|--|----------|
| B. | i) | Classify and summerize the working principles of a LC filter with suitable diagram and mathematical equations. | 8 |
| | ii) | Define inductive reactance. | 2 |
