



University of Engineering & Management, Kolkata

Term - II Examination, October - November, 2021

Programme Name: B.Tech in Computer Science

Semester: 5th

Paper Name: Analog Electronic Circuits

Paper Code: ESC 502

Full Marks:100

Time: 3 hours

GROUP A (20 Marks)

Answer the following questions. Each question is of 2 marks.

- | | | | |
|----|-------|--|---|
| 1. | i) | Relate the necessity of Amplifiers in Electronic devices | 2 |
| | ii) | Classify the types of series and shunt regulators. | 2 |
| | iii) | Sketch the importance of DC load line in Transistors | 2 |
| | iv) | Illustrate the four hybrid parameters of a two port network. | 2 |
| | v) | Point out the topologies for negative feedback amplifier. | 2 |
| | vi) | Explain Barkhausen Criterion. | 2 |
| | vii) | Explain the basic amplifiers in feedback topology | 2 |
| | viii) | Discuss about input biased current | 2 |
| | ix) | Illustrate Multivibrator | 2 |
| | x) | Show the working principle of a Scmitt Trigger | 2 |

GROUP B (30 Marks)

Answer the following questions. Each question is of 5 marks.

- | | | |
|-------|--|---|
| 2. | Sketch the diagram of a Series regulator and explain its operation | 5 |
| 3. | Judge biasing of BJT and defend need for biasing. | 5 |
| 4. | Discuss Barkhausen criterion and its function. | 5 |
| 5. A. | Illustrate CMRR in Op Amp | 5 |

OR

- | | | |
|----|------------------------------------|---|
| B. | Show the Virtual ground in Op -Amp | 5 |
|----|------------------------------------|---|

6. A. Analyze the significance of infinite input impedance in Op Amp 5

OR

- B. Demonstrate the function of Integrator Circuit in Op Amp 5

7. A. Sketch the Square wave signal. 5

OR

- B. Sketch bistable multivibrator. 5

GROUP C (50 Marks)

Answer the following questions. Each question is of 10 marks.

8. i Sketch and explain full wave center tapped rectifier circuit. 5
 ii) Reframe mathematically the ripple factor of a half wave rectifier is 1.21. 5

9. i) Sktch with suitable circuit diagram the input and output characteristics of a Transistor working in CB mode. 5
 ii) Analyze the expression for current gain 5

10. A. i) Reframe Oscillator with respect to Barkhausen Criterion. 5
 ii) Sketch the function of tank circuit and explain its operation 5

OR

- B. i) List the ideal characteristics of op-amp 5
 ii) Design a subtractor circuit using OPAMP 5

11. A. i) Sketch op-amp voltage follower circuit & explain it. 5
 ii) Construct and label an inverting amplifier circuit for a voltage gain of 10. 5

OR

- B. For a non-inverting amplifier where $R_L=10\text{ k}\Omega$ and $V_1=1\text{ V}$. Determine (a) V_0 , (b) gain, (c) I_L , (d) load current I_L and (e) output current I_0 . take standard Op Amp Non inverting amplifier as example 10

12. A. i) Design a differential amplifier using Op Amp and explain its operation. 5
 ii) State the requirements of differential amplifier for making Op Amp. 5

OR

- | | | | |
|-----------|------------|--|---|
| B. | i) | Distinguish differences between astable and monostable multivibrators. | 5 |
| | ii) | State applications of Multivibrators. | 5 |
