

ABHISHEK SHARMA

Year : Third

Section : "3I"

Class Roll No.: 01

Enrolment No.: 12019009001127

ANALOG ELECTRONICS CIRCUIT LAB

DAY 2

ASSIGNMENT 2

DATE : 20.07.2021

Platform Used : Multisim Online Live Simulator


**UNIVERSITY OF ENGINEERING & MANAGEMENT, KOLKATA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING**

A. Draw the circuit of a Half wave Rectifier without using the capacitor.


Requirements :

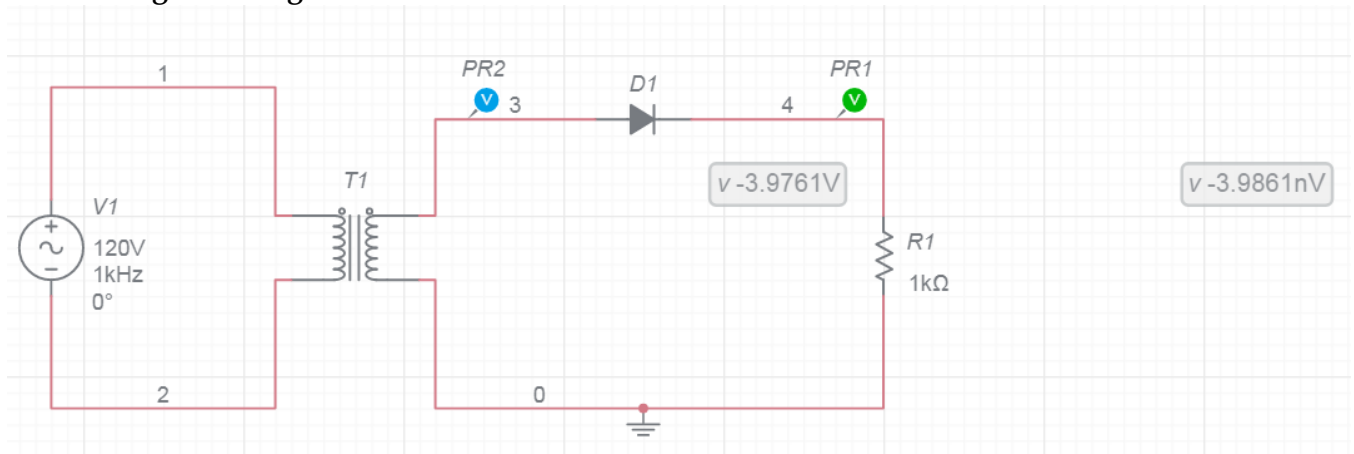1. AC Power Source [120 V]
2. Diode
3. Resistor [1k Ω]
4. Transformer [1P1S]
5. Ground
6. Voltmeters

Circuit Diagram using Multisim Online Live Simulator :



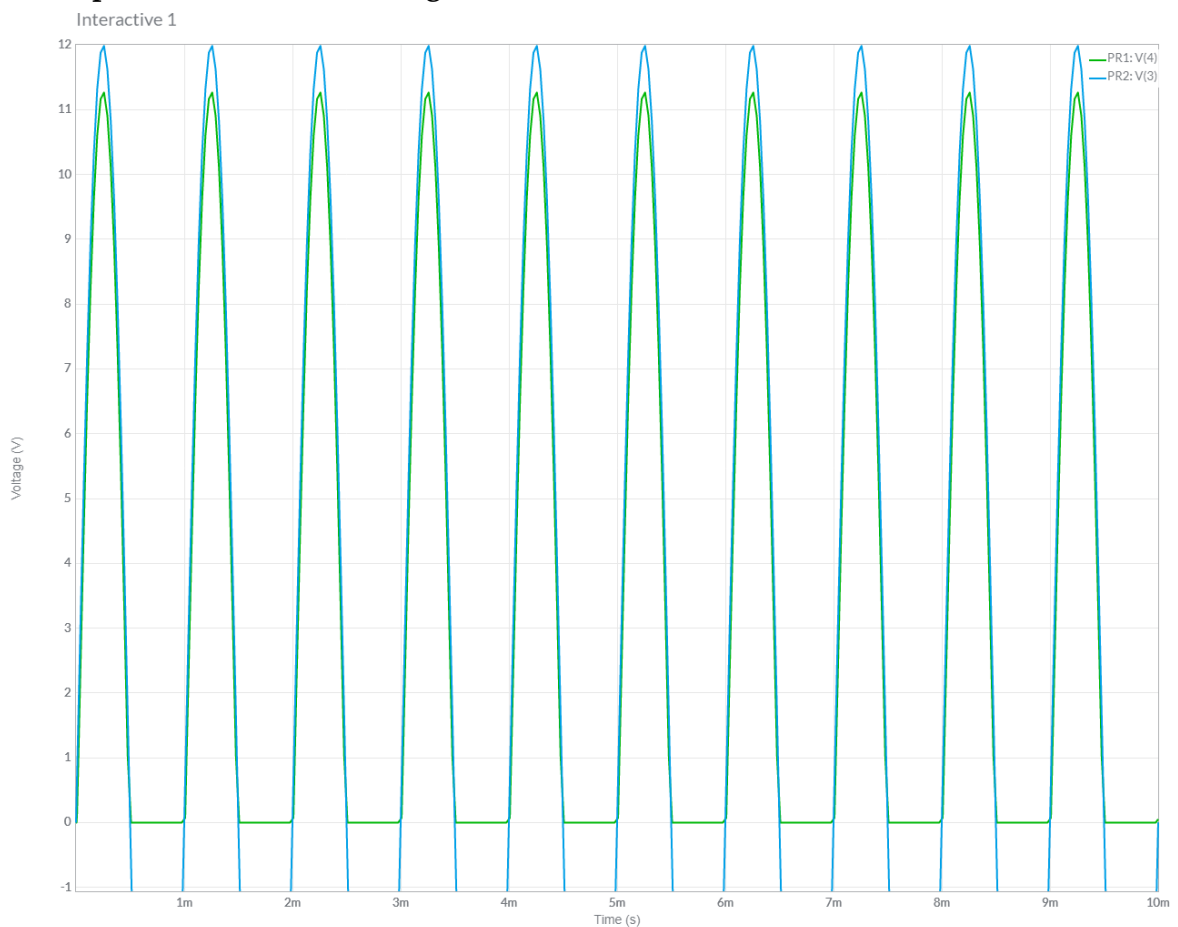Graphical Representation of the Voltage :




B. Draw the circuit of a Half wave Rectifier using the capacitor of different values and analyze.


Requirements :

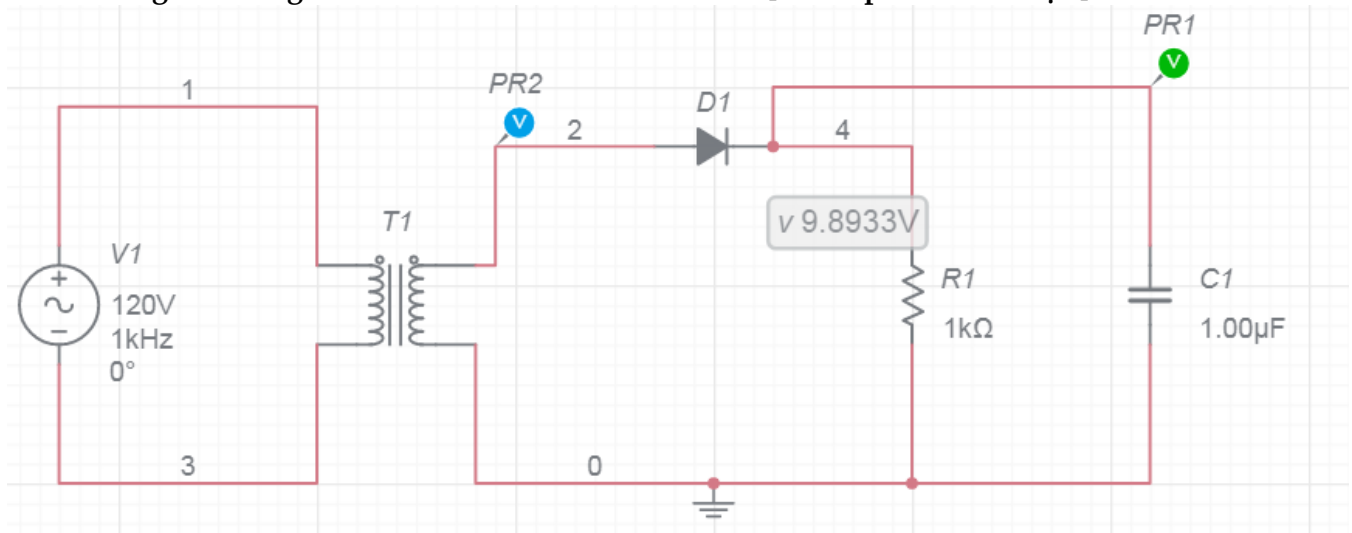1. AC Power Source [120 V]
2. Diode
3. Resistor [1k Ω]
4. Transformer [1P1S]
5. Ground
6. Voltmeters
7. Capacitors [1 μ F, 4.5 μ F and 10 μ F]


Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of 1 μ F]



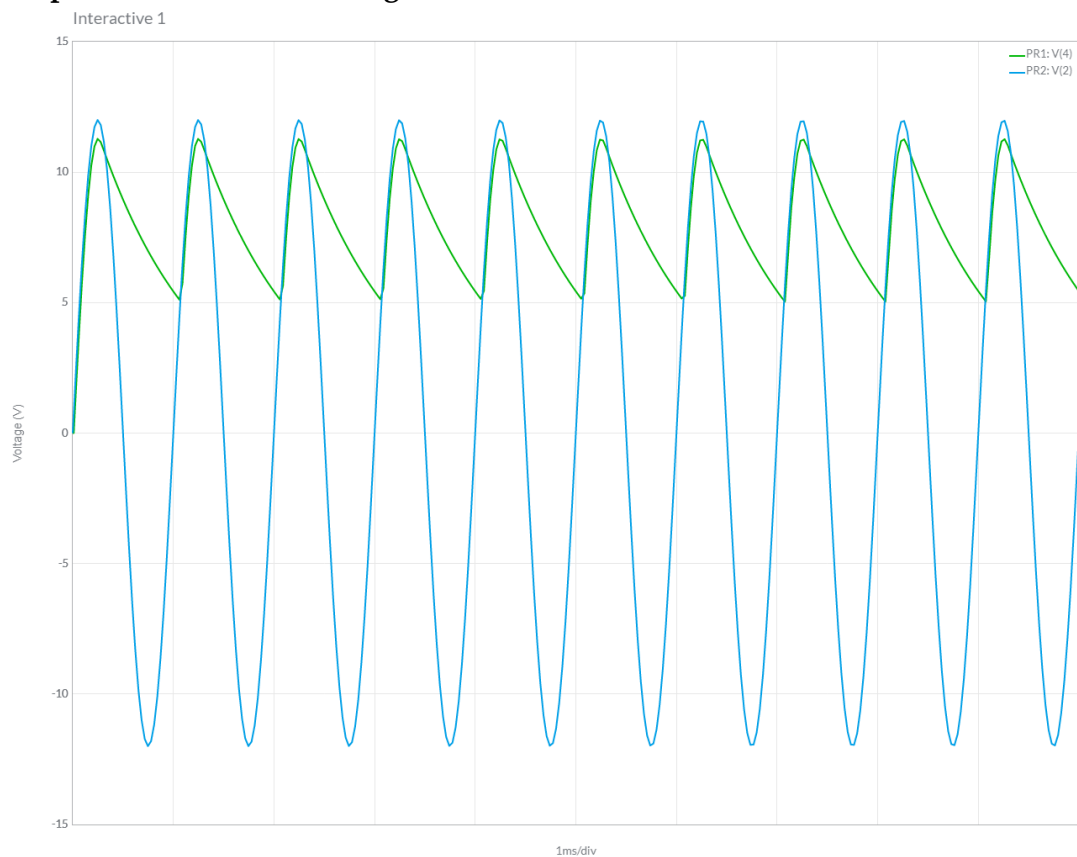
Graphical Representation of the Voltage :



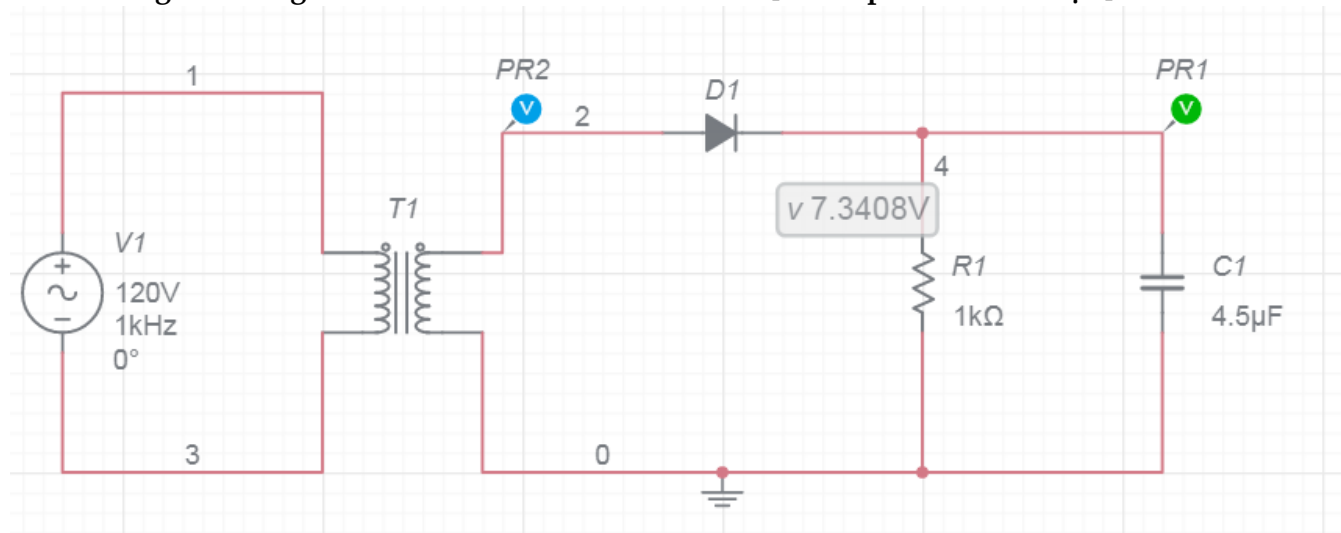
Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of $4.5\mu\text{F}$]



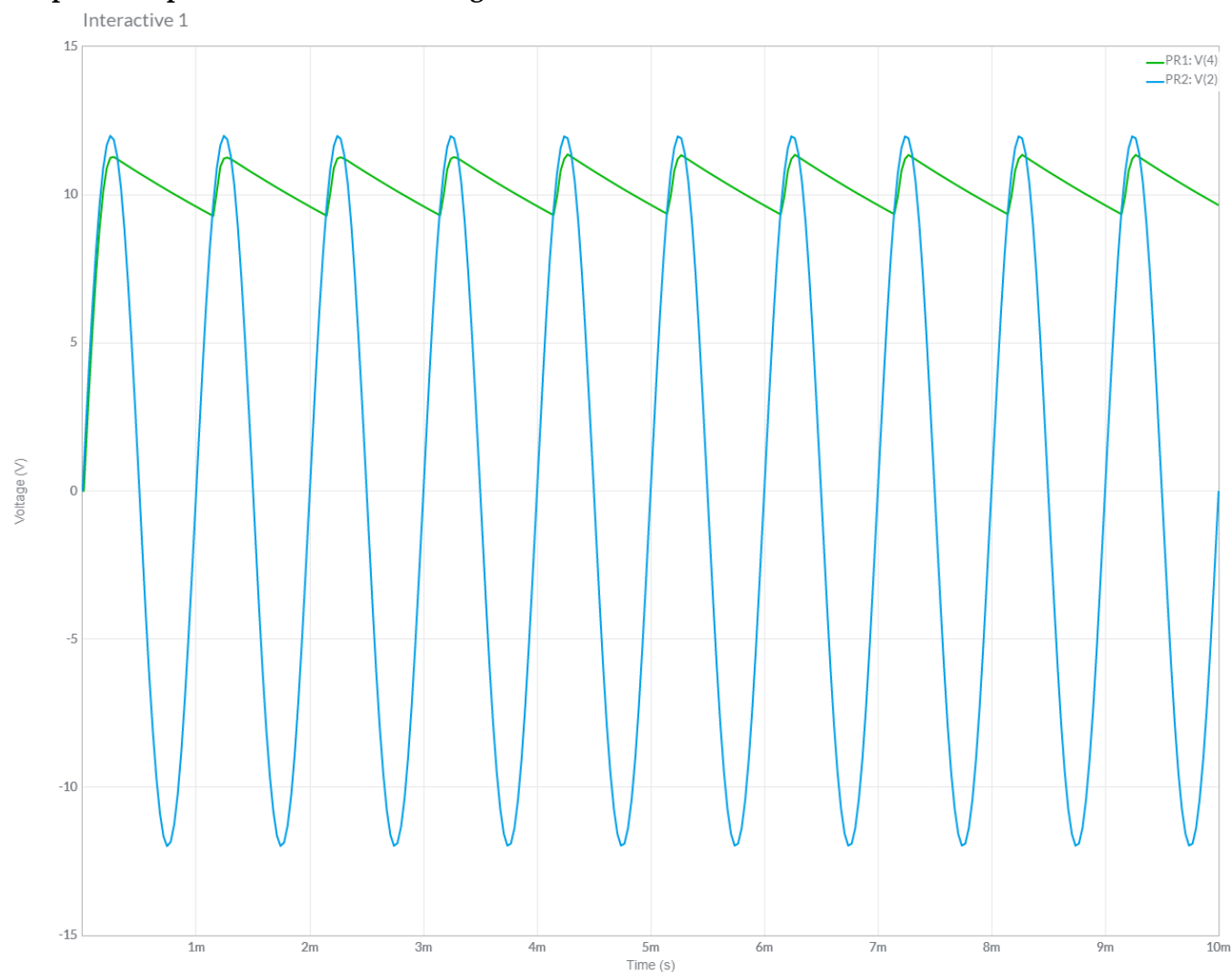
Graphical Representation of the Voltage :



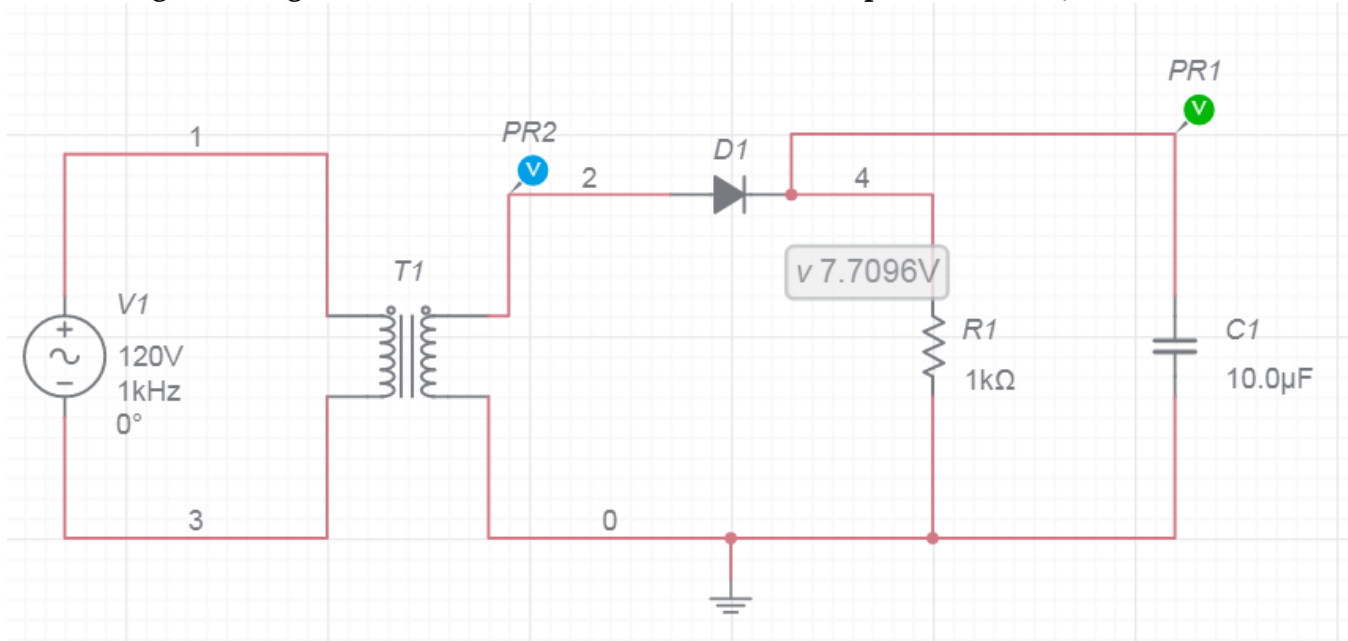Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of 10 μ F]



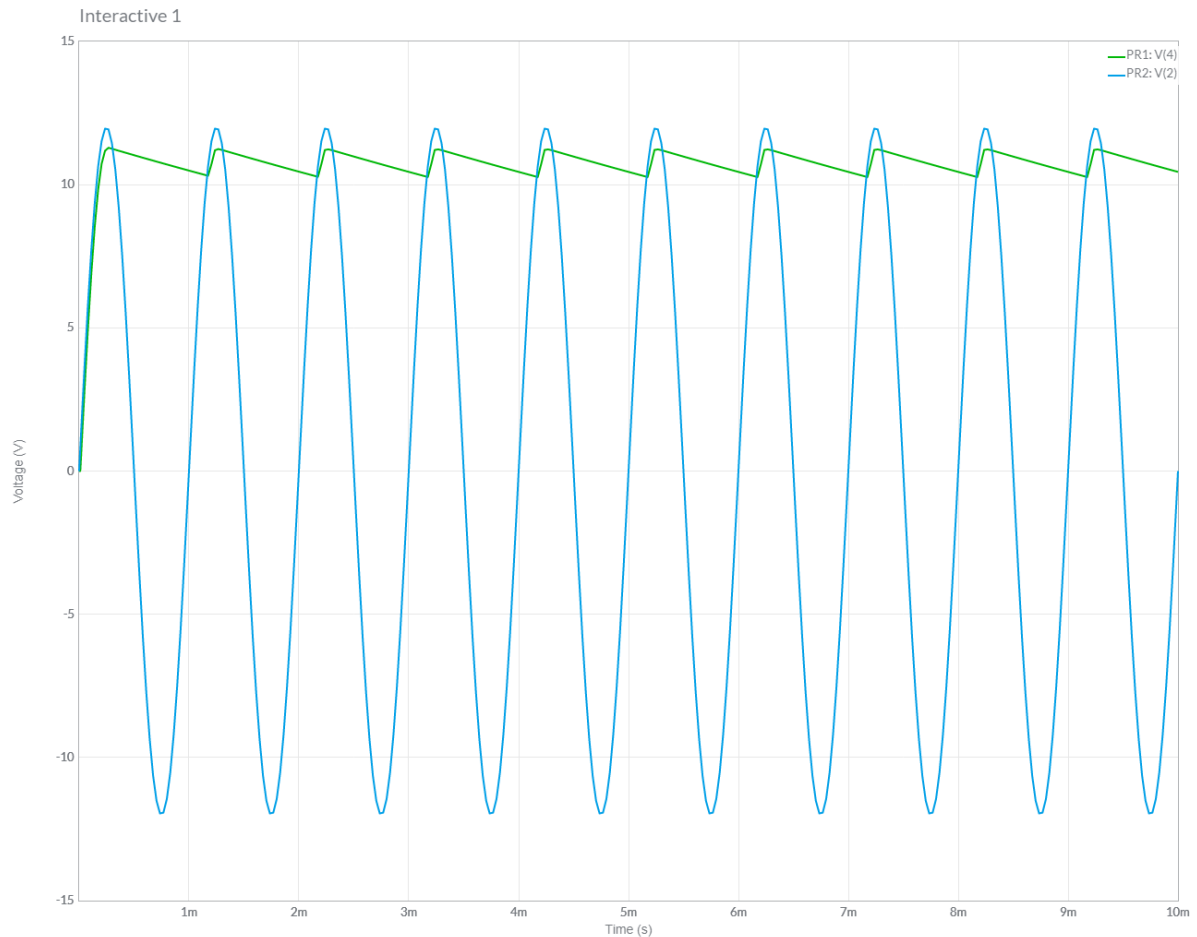Graphical Representation of the Voltage :



Observation :


As the capacitance values increase, the AC voltage gets more bypassed by the capacitor and the resistor is having the pure DC voltage through the line. That's why the graph is considering to be like that and the voltage becomes more DC rather tends to be pure DC.

C. Draw the circuit of a Full wave Rectifier without using the capacitor.


Requirements :

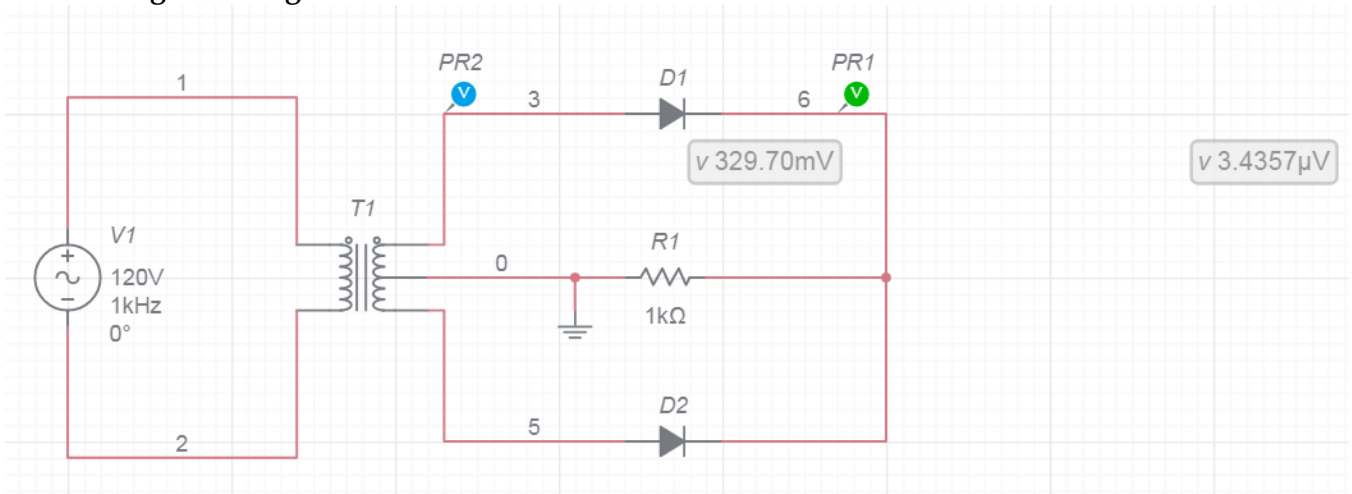1. AC Power Source [120 V]
2. Diodes
3. Resistor [1k Ω]
4. Transformer [1P1S Centre Tapped]
5. Ground
6. Voltmeters

Circuit Diagram using Multisim Online Live Simulator :



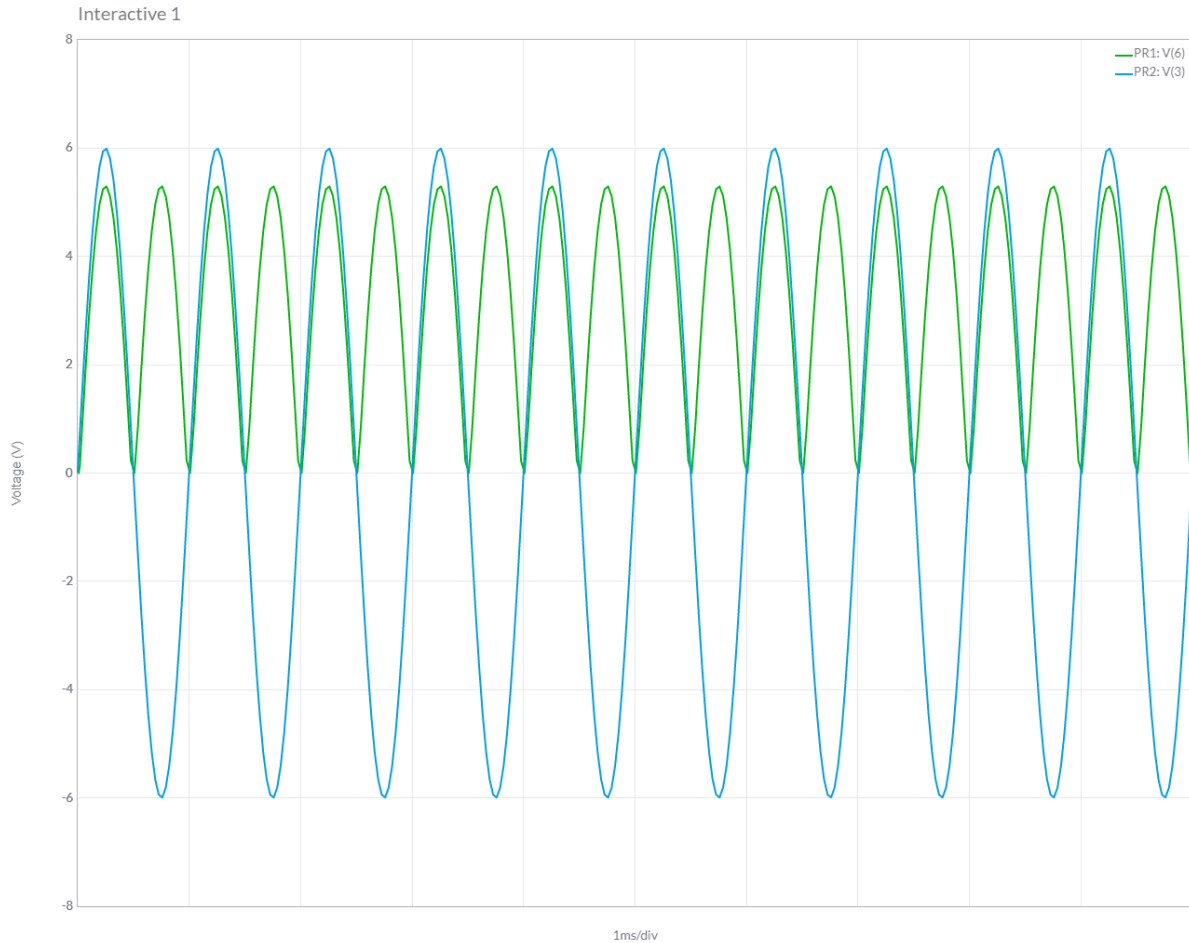Graphical Representation of the Voltage :




D. Draw the circuit of a Full wave Rectifier using the capacitor of different values and analyze.


Requirements :

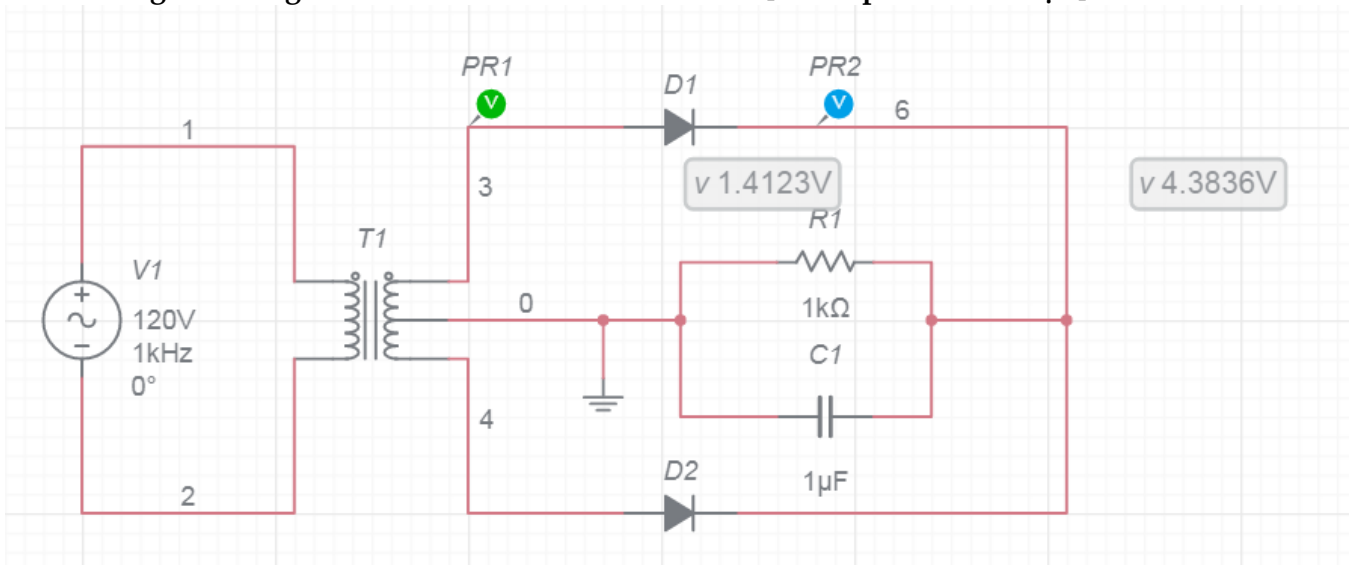1. AC Power Source [120 V]
2. Diodes
3. Resistor [1k Ω]
4. Transformer [1P1S Centre Tapped]
5. Ground
6. Voltmeters
7. Capacitors [1 μ F, 5 μ F and 10 μ F]


Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of 1 μ F]



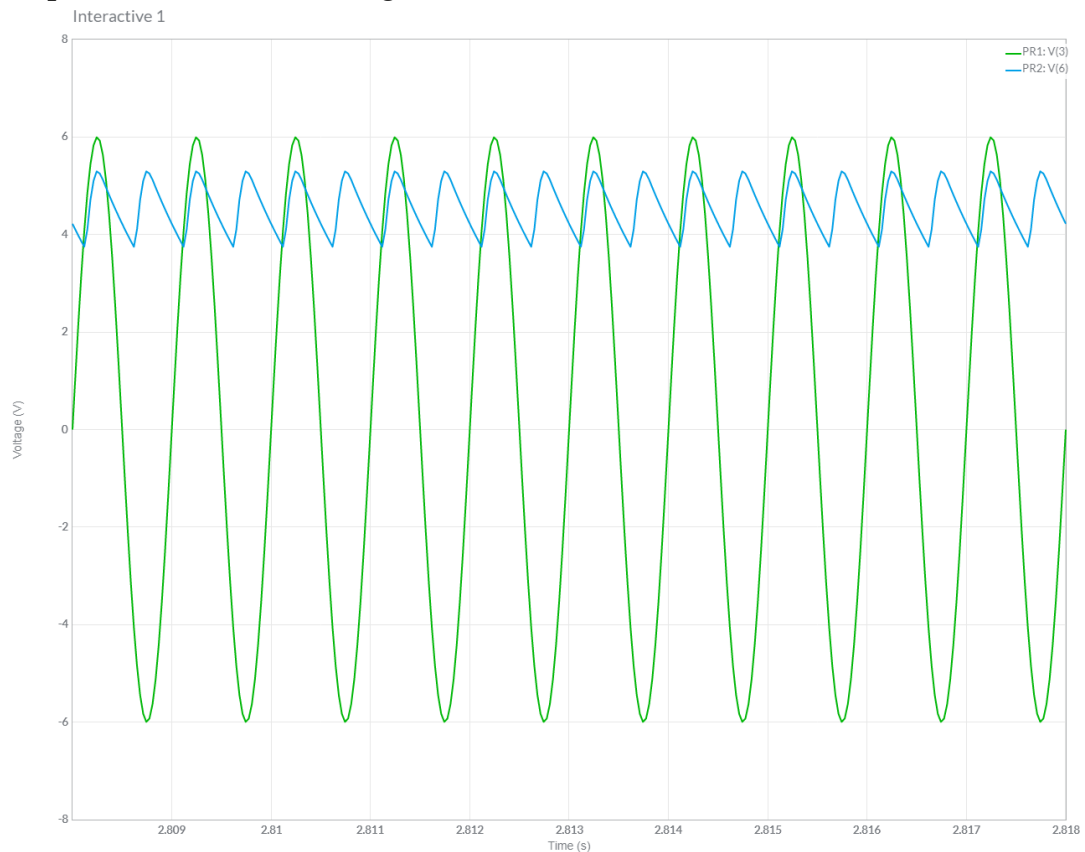
Graphical Representation of the Voltage :



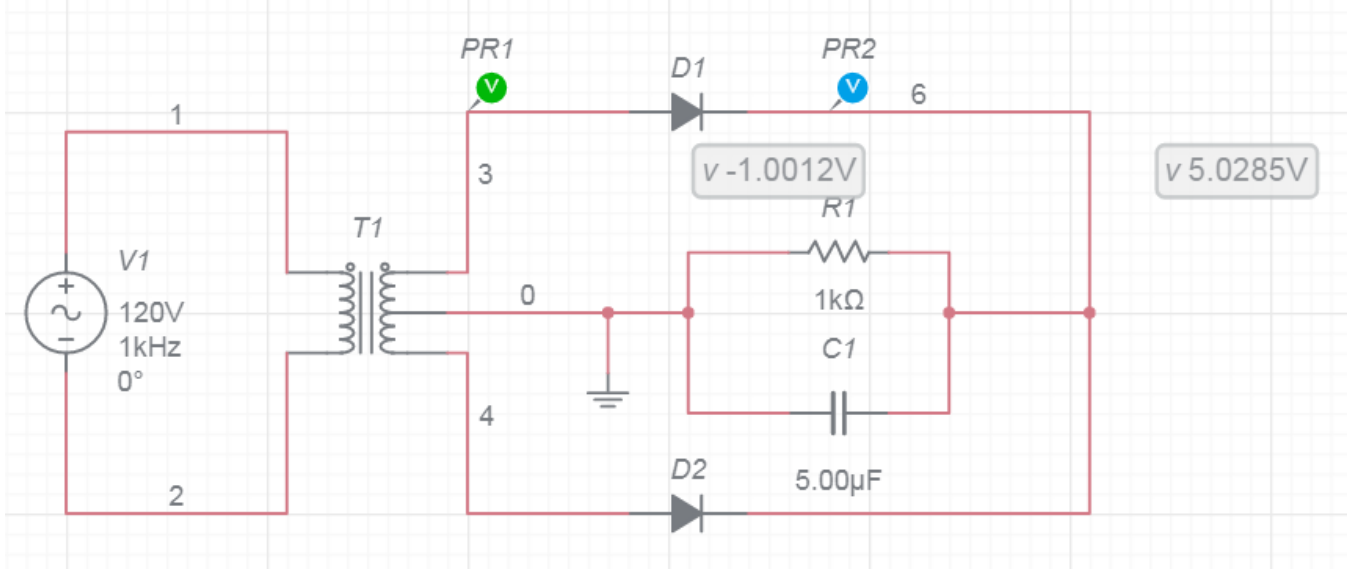
Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of 5μF]



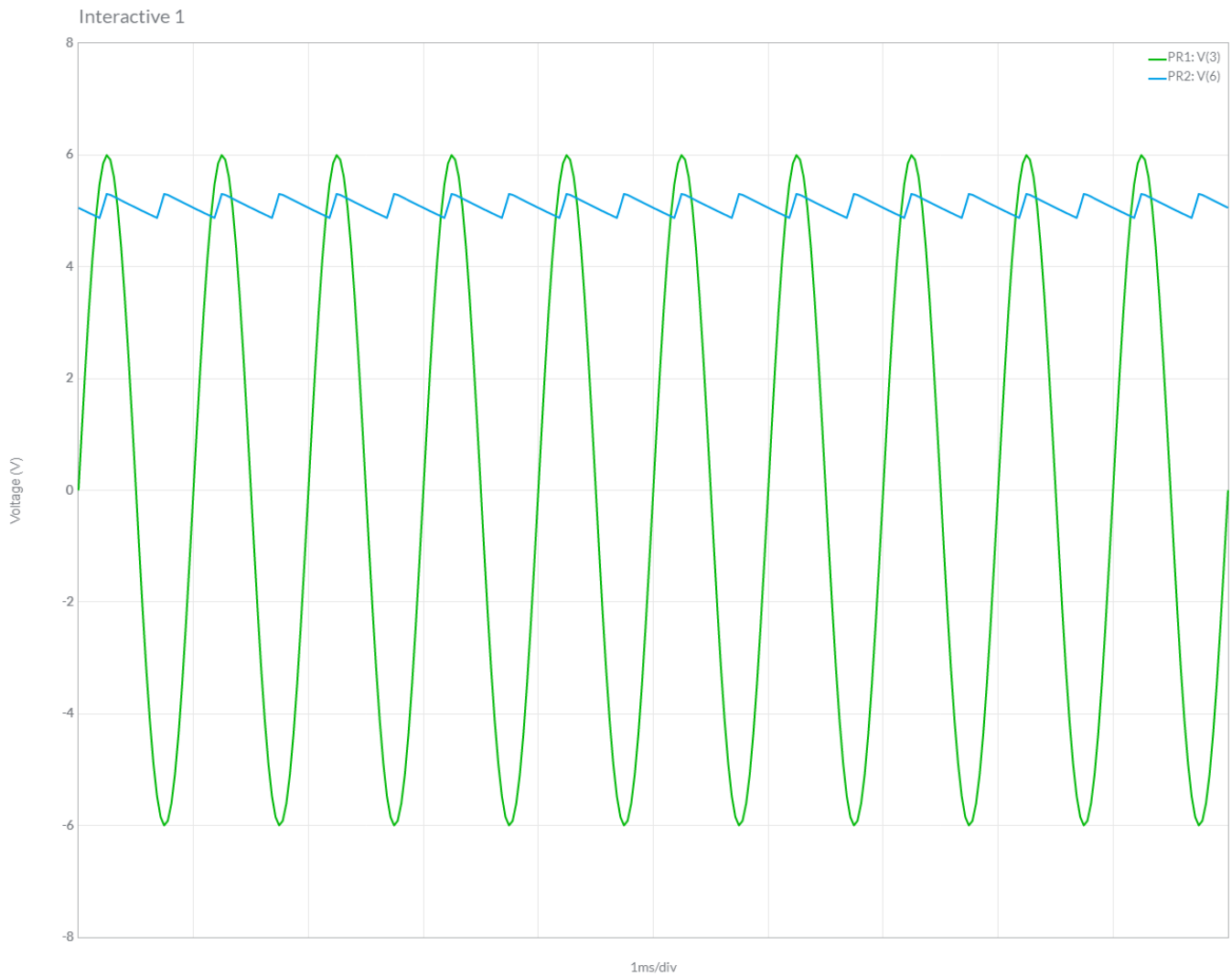
Graphical Representation of the Voltage :



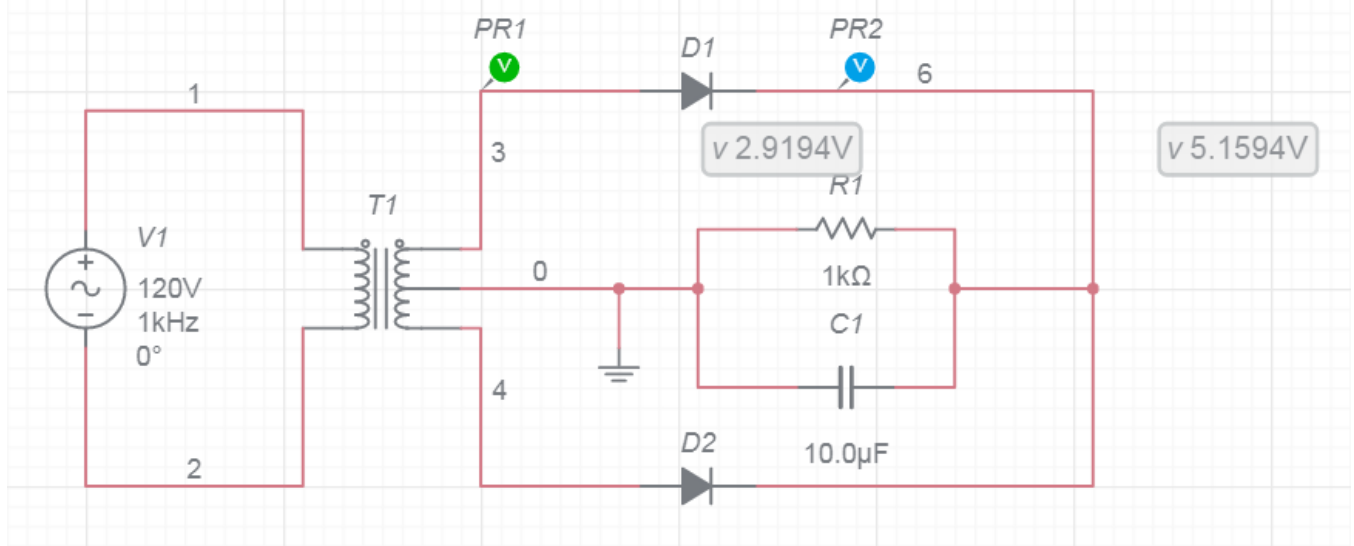Circuit Diagram using Multisim Online Live Simulator : [For Capacitance of 10 μ F]



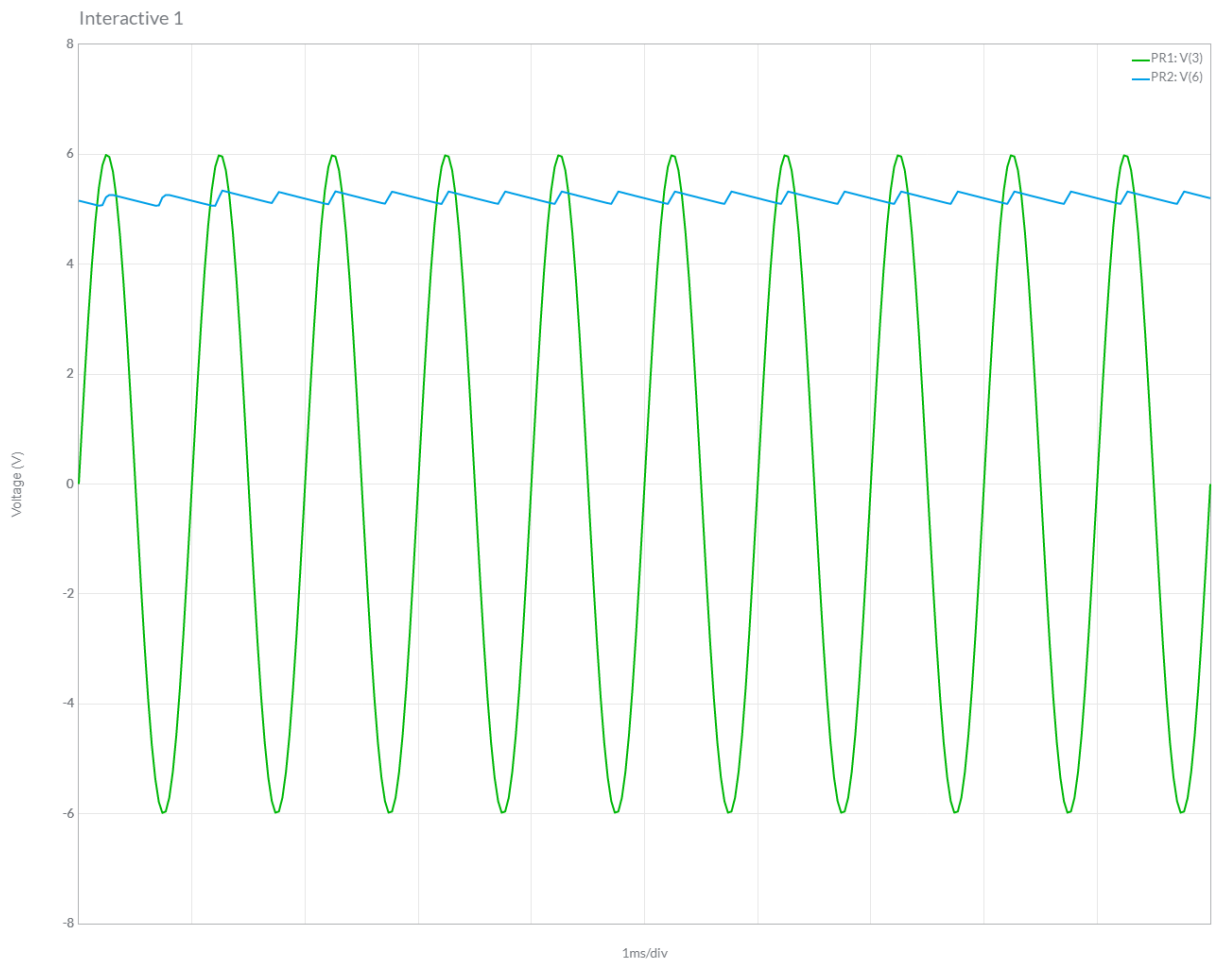Graphical Representation of the Voltage :



Observation :

As the capacitance values increase, the AC voltage gets more bypassed by the capacitor and the resistor is having the pure DC voltage through the line. That's why the graph is considering to be like that and the voltage becomes more DC rather tends to be pure DC.

For both the half and full wave rectifiers we have seen that capacitance decreased the ripple factor and make the voltage tends to be pure DC by increasing the value of the C.