

ABHISHEK SHARMA

CS THIRD YEAR, SECTION : "I", ROLL NO.: 01

ENROLLMENT NO.: 12019009001127


ANALOG ELECTRONICS LAB CLASS ASSIGNMENT [Viva Voce]

DATE : 22.10.2021


UNIVERSITY OF ENGINEERING AND MANAGEMENT, KOLKATA

Q1. Add 5V, 3V and 2V using non-inverting terminal.

Circuit Diagram :

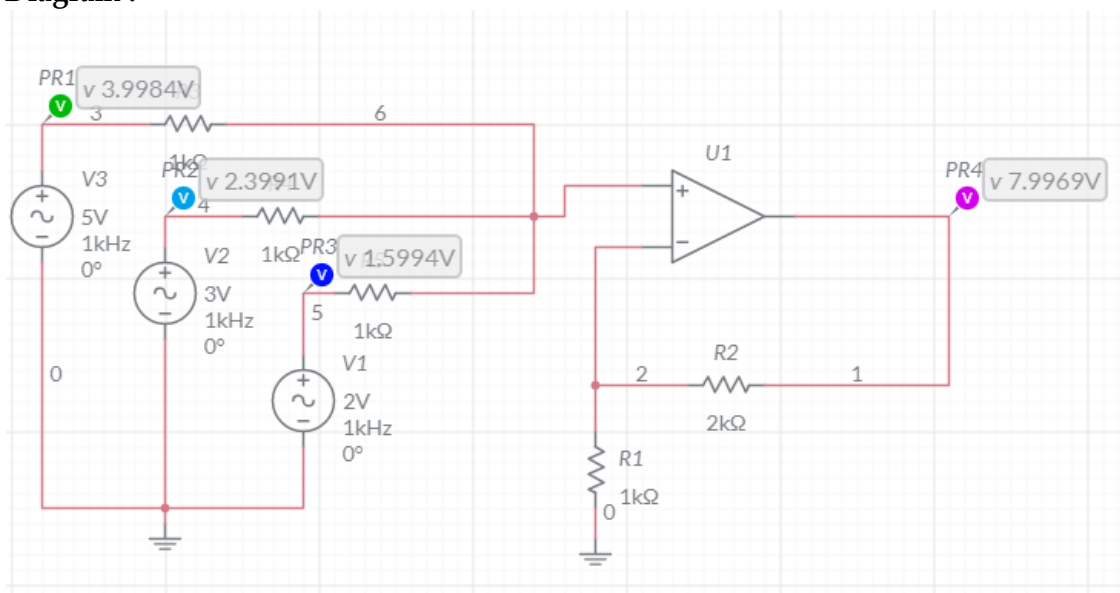


Graph :

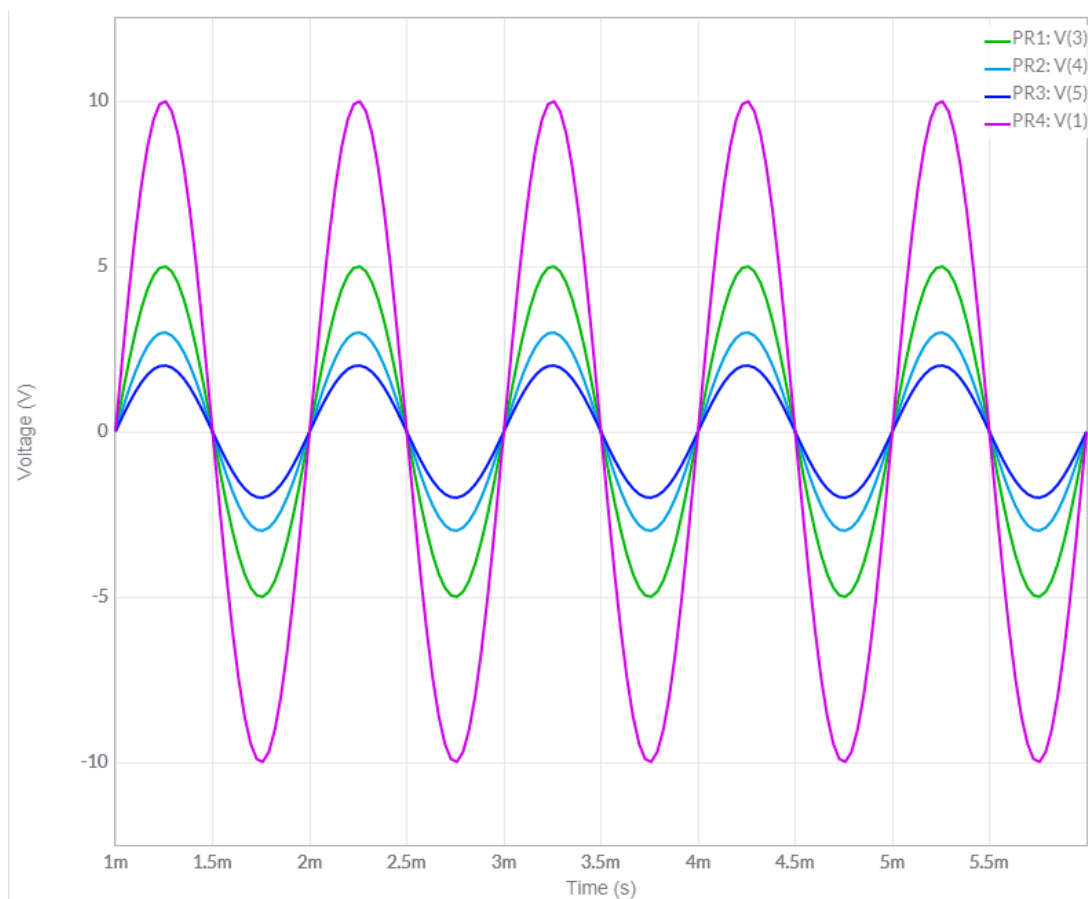


Q2. Add 1V, 2V and 8V using inverted terminal.

Circuit Diagram :

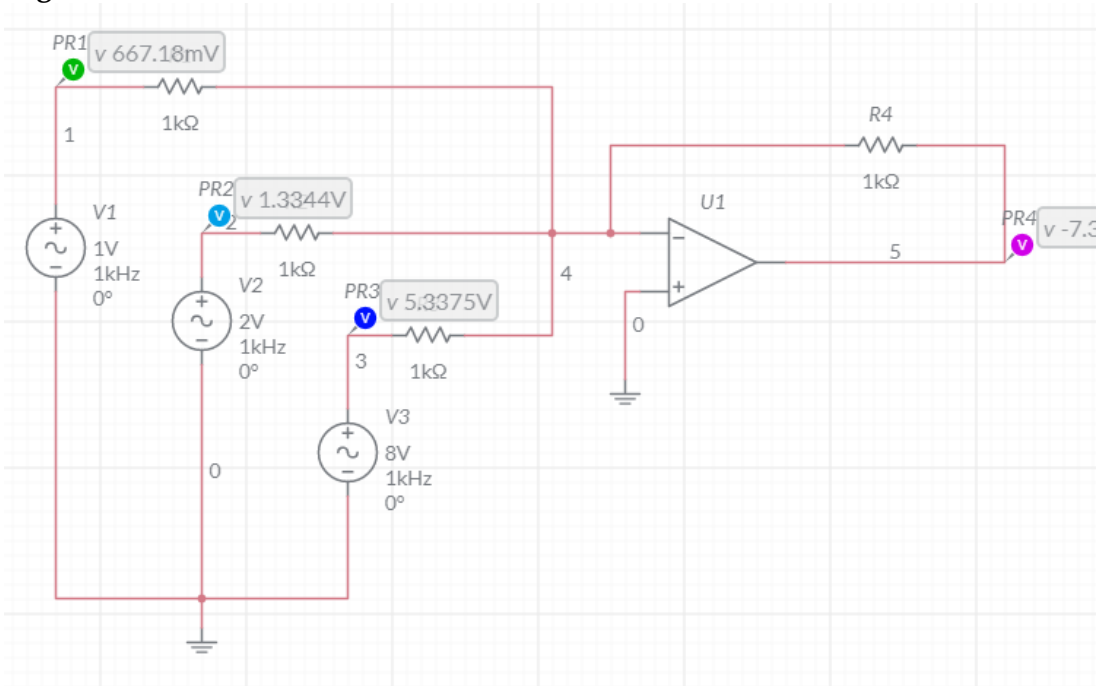


Graph :

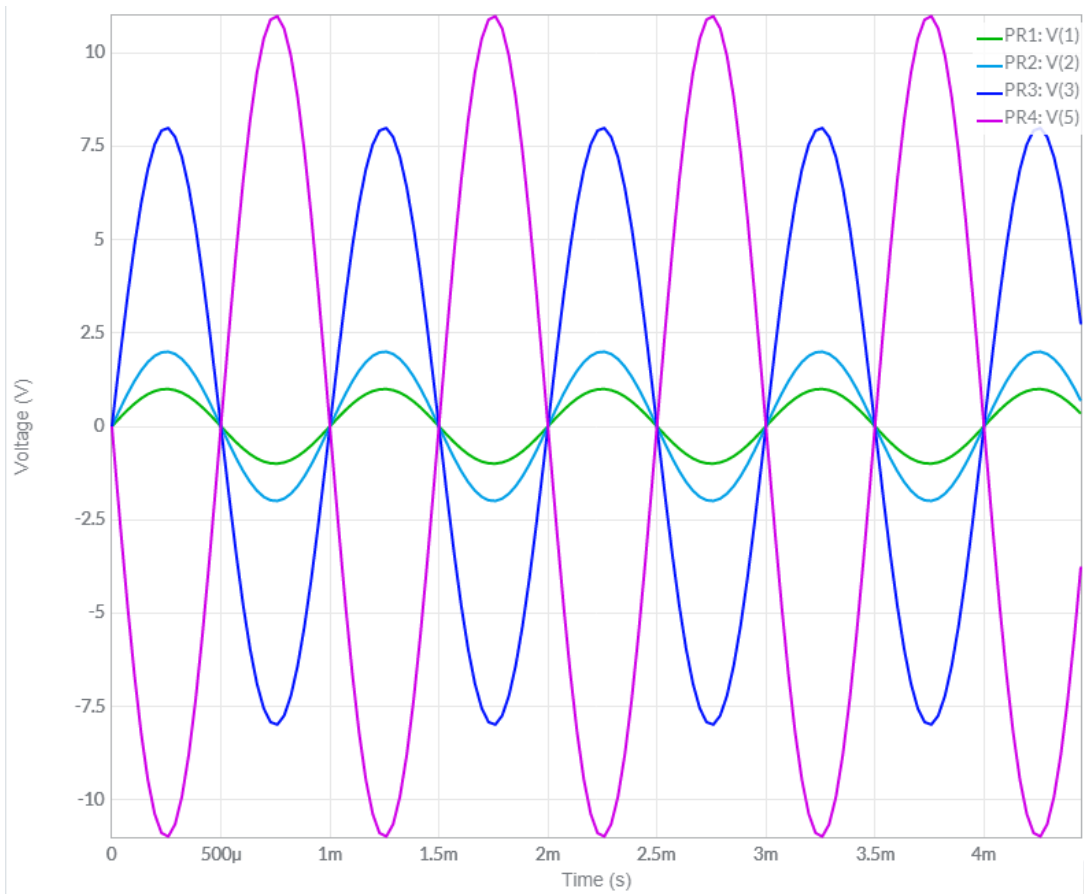


Q3. Perform the following addition: $0.5 \times V1 + 2 \times V2$. Here V1 and V2 are AC voltages ranging from 6V to -6V and 2V to -2V respectively.

Circuit Diagram :

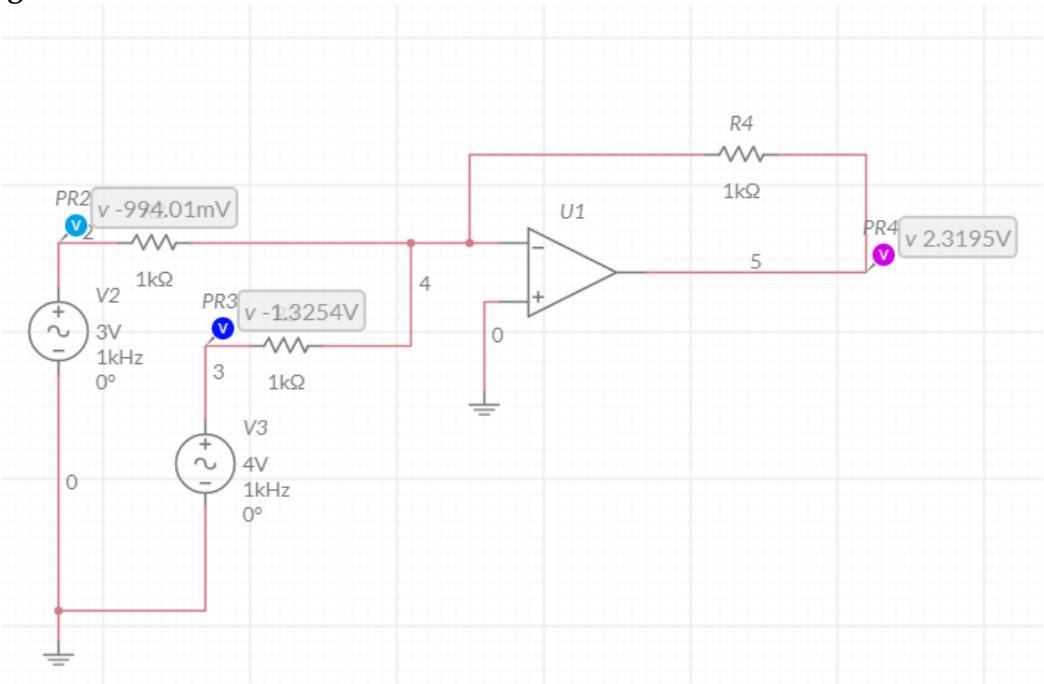


Graph :

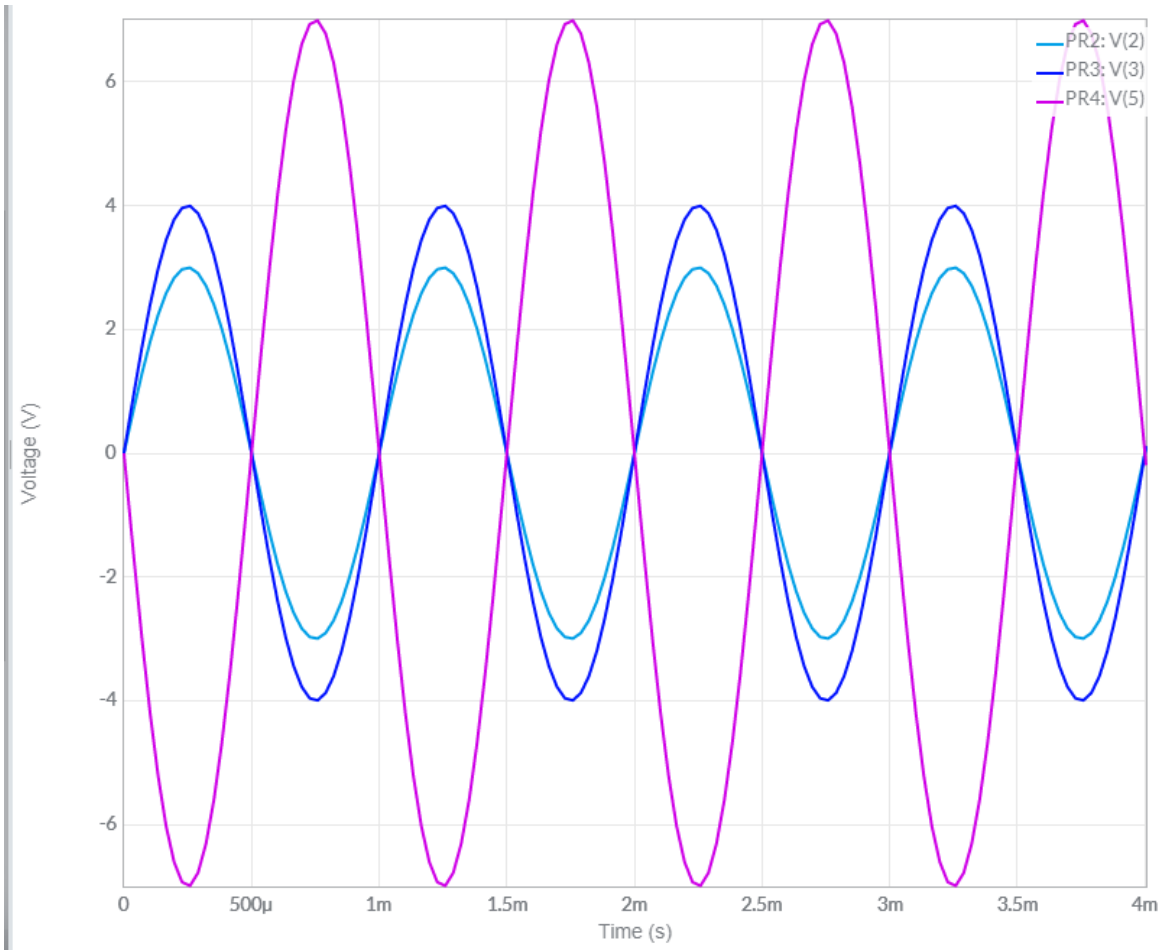

Q4. Perform subtraction of V1 and V2 (i.e. V1 - V2). Here V1 and V2 are Av voltages ranging from 3V to -3V and 2V to -2V respectively.

Circuit diagram:

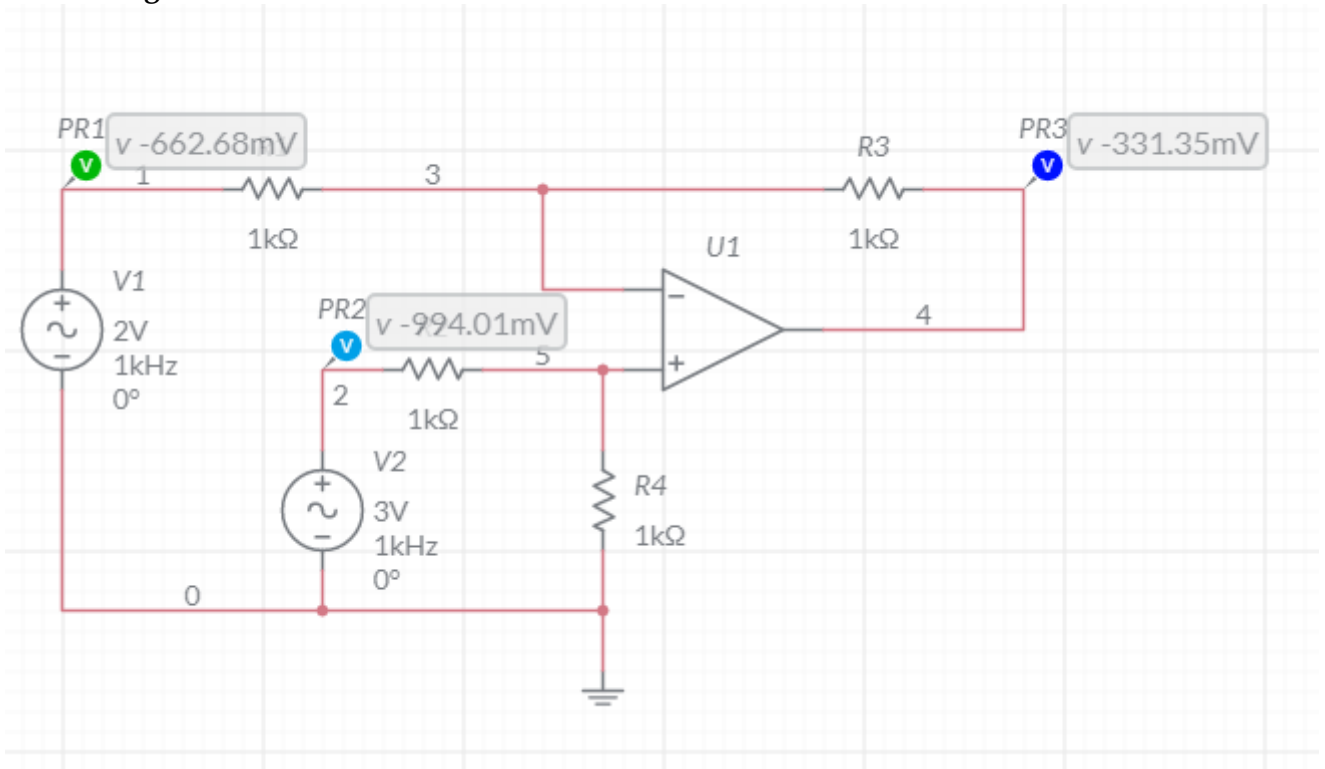

Graphical representation:

